


EE228 – HW2 Report
4-bit Flash ADC & DAC
using ideal components & VerilogA

Muhammad Aldacher
Student ID: 011510317


(1)

Using Ideal Components


Comparator

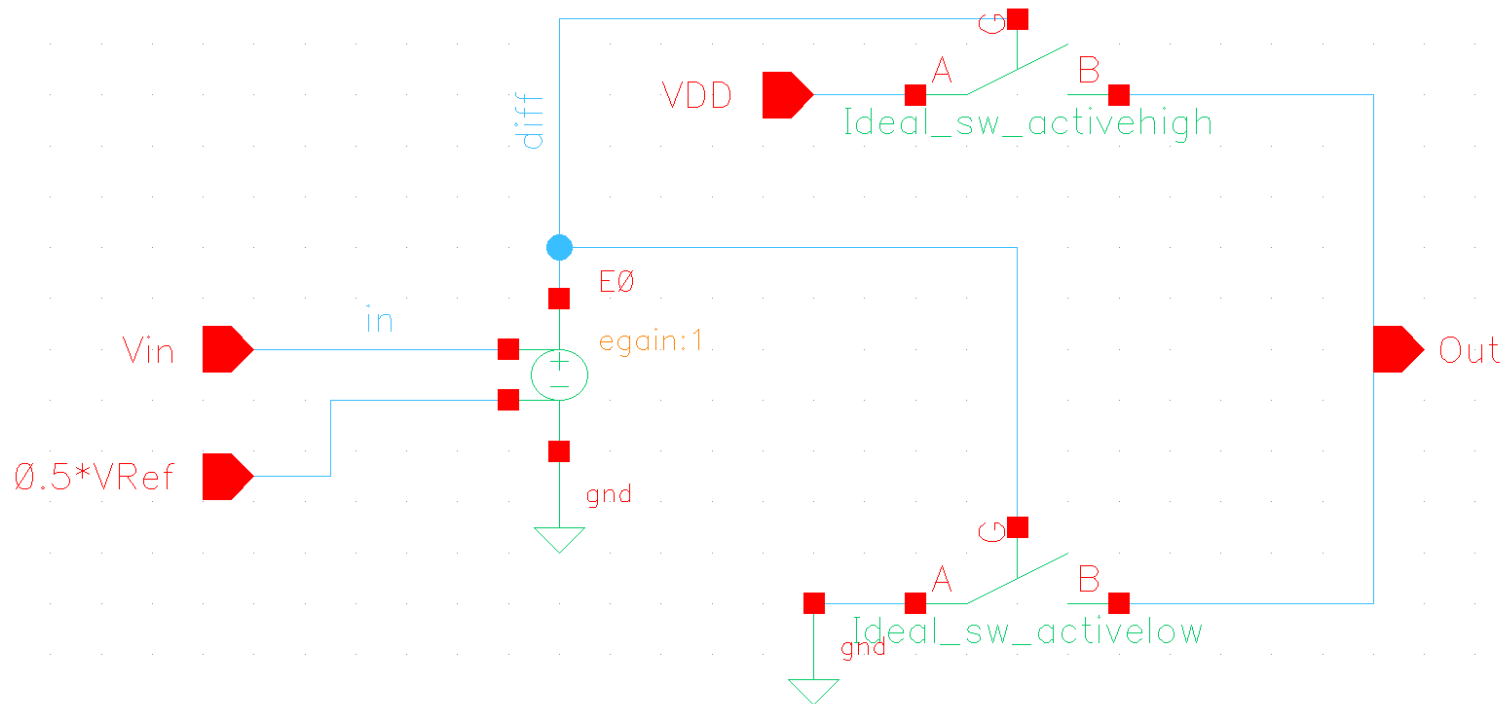

Clocked Comparator

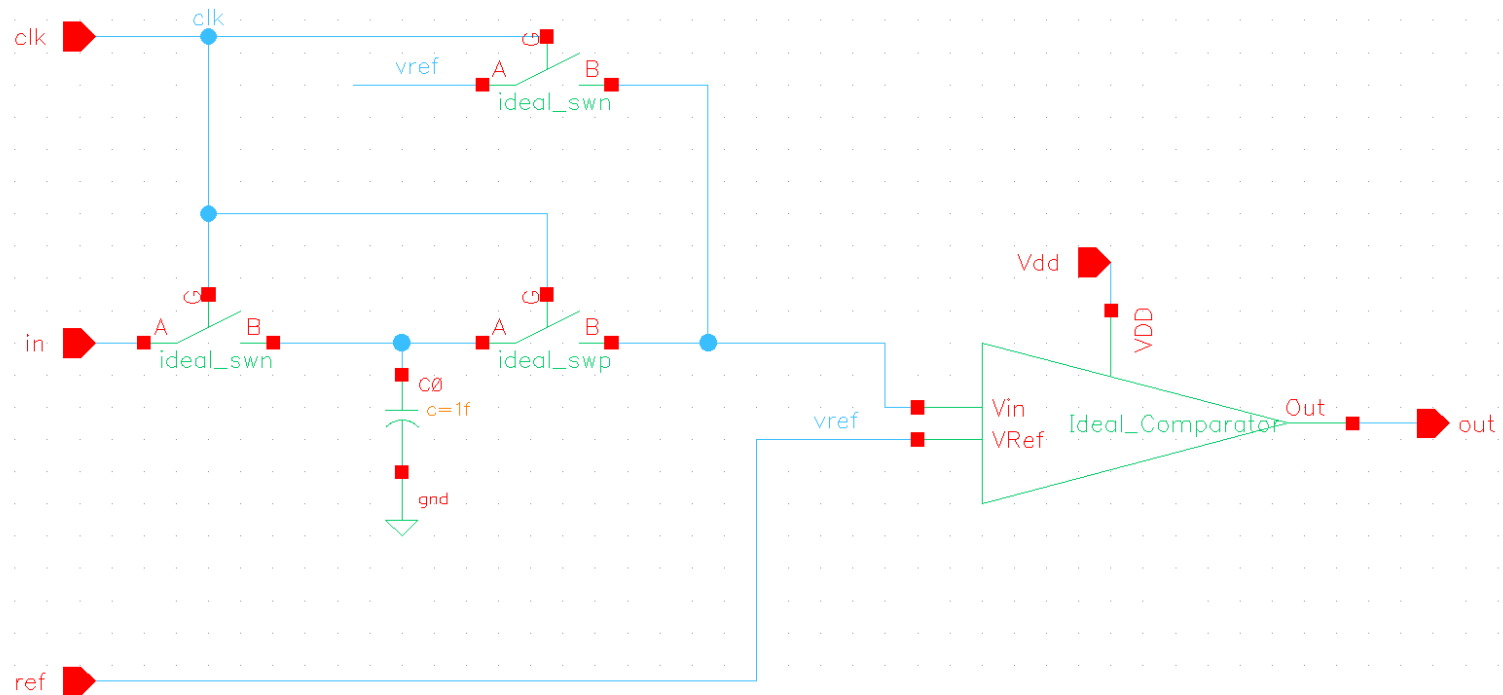


Resistive Ladder & Clocked Comparators

 


Logic Gates


Inverter

 


NAND

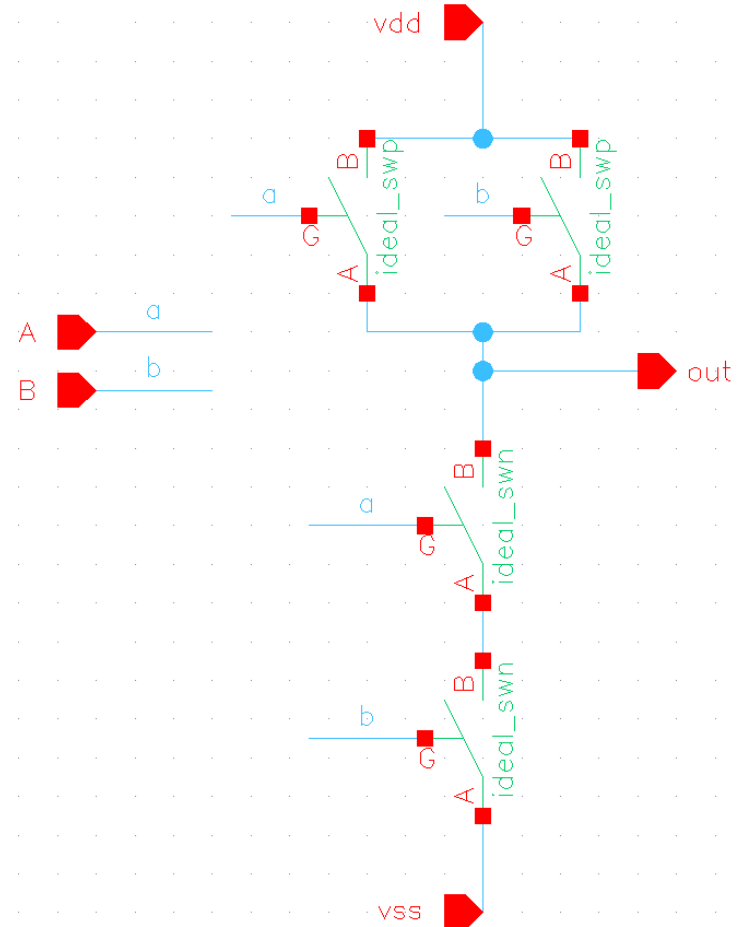

 
Thermometer-to-Binary Encoder (ROM Encoder)




4-bit Flash ADC

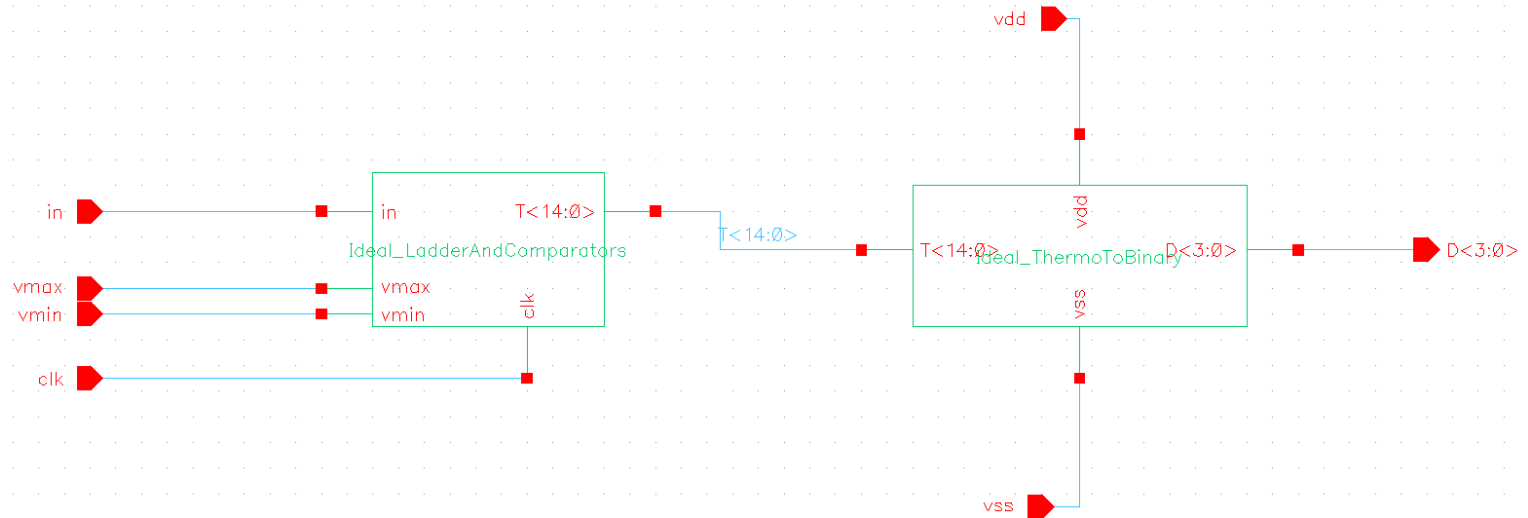

4-bit DAC

 


Testbench for the ADC & the DAC

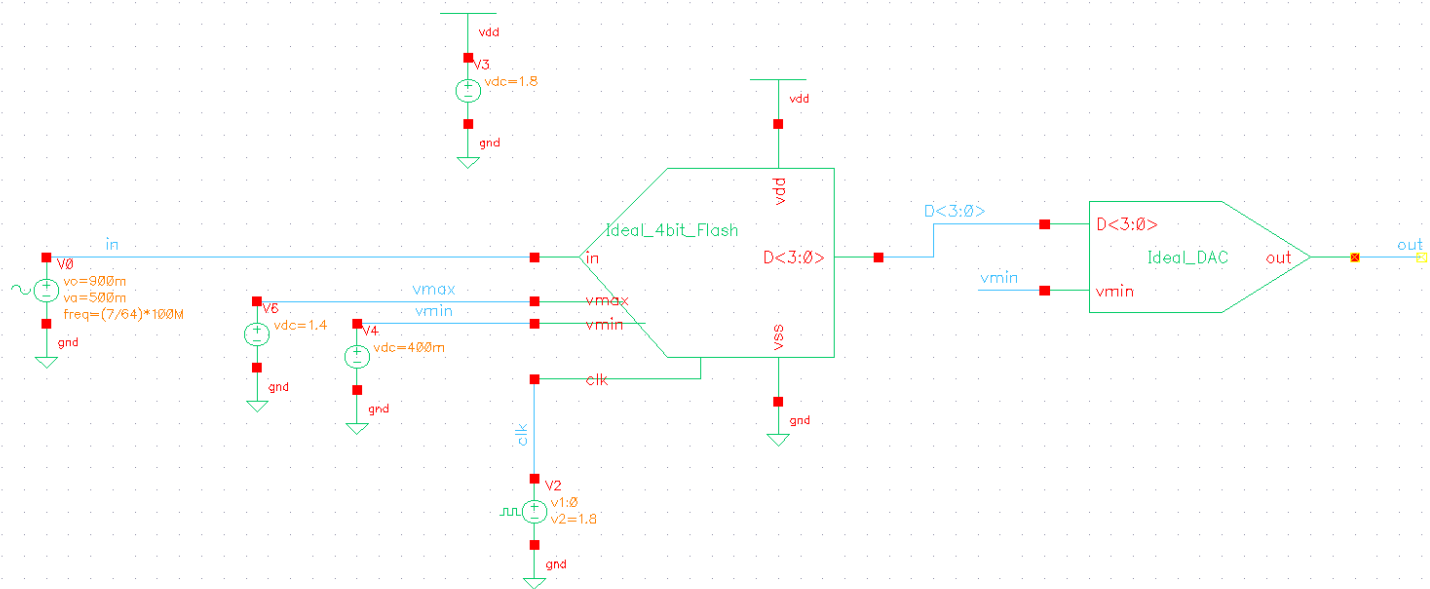

Test Results: Analog Waveforms

Transient Response

Tue Feb 20 23:48:41 2018

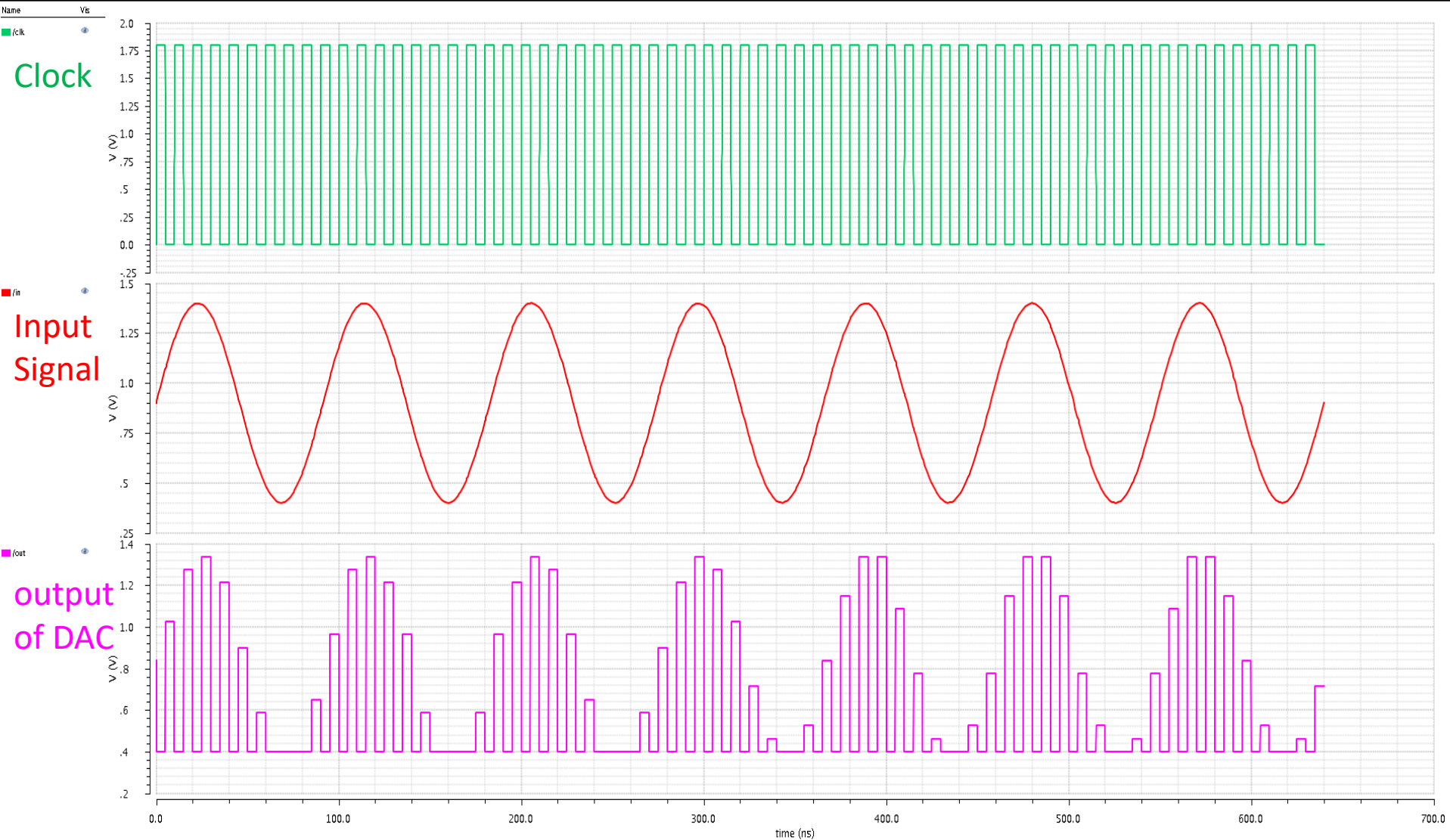


Test Results:

Thermometer Outputs from Comparators

Transient Response

Tue Feb 20 23:55:23 2018

 

Test Results:


Digital Outputs from Encoder

Transient Response

Name

v / D<3>; tan (V)

D<3>

 


v / D<2>; tan (V)

D<2>




v / D<1>; tan (V)

D<1>

 


v / D<0>; tan (V)

D<0>

 


Test Results: DFT from Cadence

 dft(v("/out" 7result "tran") 0 640n 64 "Rectangular" 1 "default")




 Matlab: Output Waveform reconstructed from sampled data



Matlab:

 Output spectrum using DFT (from $N = 1 \rightarrow 33$)




(2)

Using VerilogA Blocks

(Using a “Ladder & Comparators” VerilogA Block)


4-bit Flash ADC & DAC

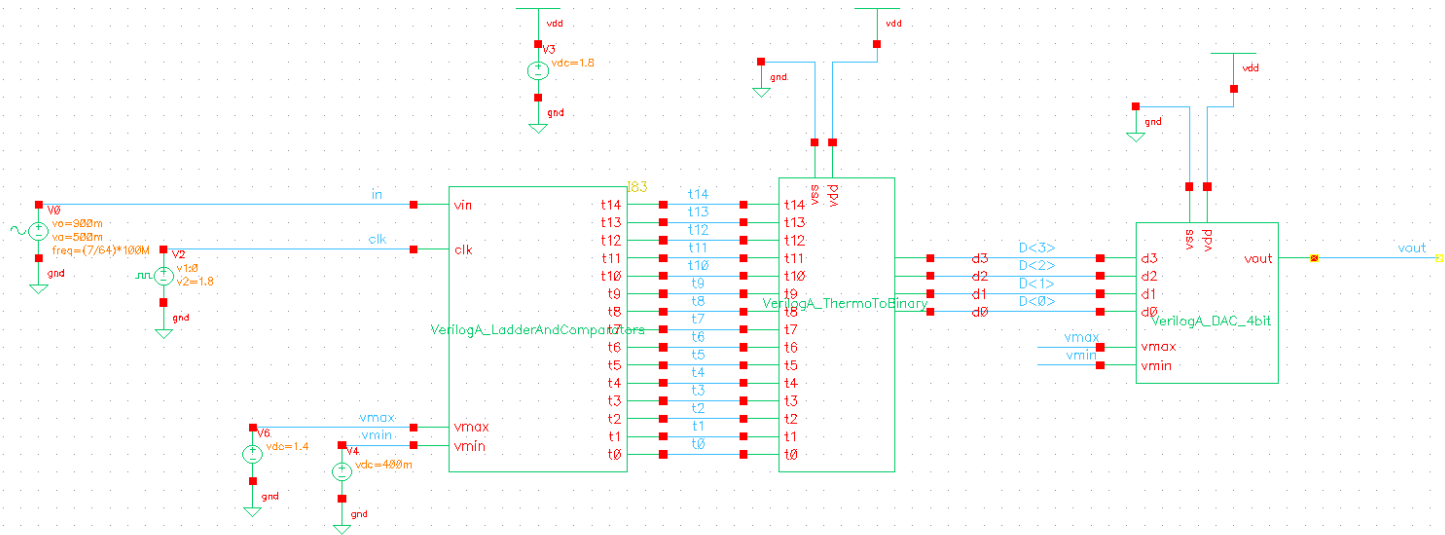

Test Results: Analog Waveforms


Transient Response

Sat Feb 24 11:38:14 2018

 

Test Results:

Thermometer Outputs from Comparators

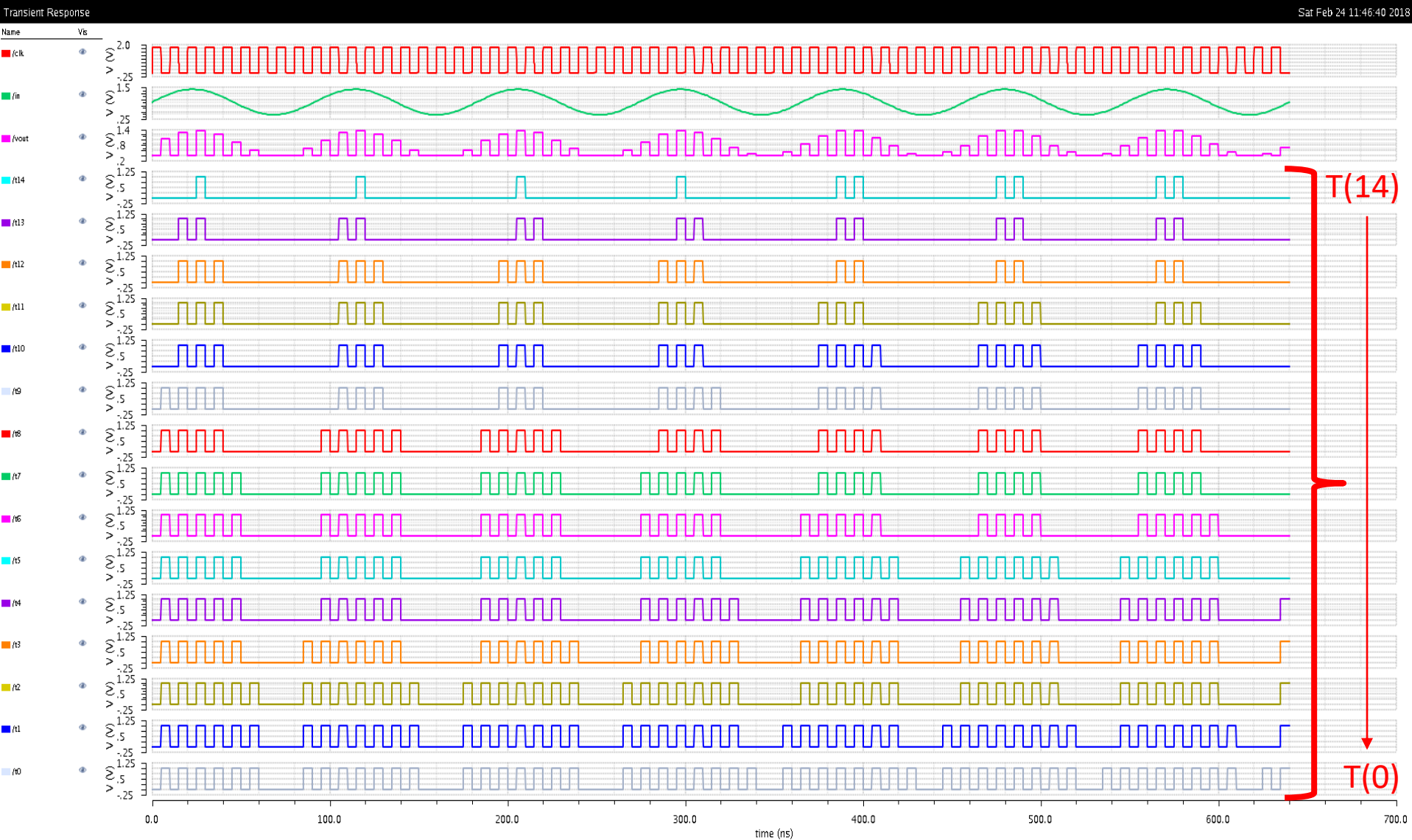

Test Results:


Digital Outputs from Encoder

Transient Response

Name


v / D<3>; tan (V)

D<3>

 


v / D<2>; tan (V)

D<2>

 


v / D<1>; tan (V)

D<1>

 

v / D<0>; tan (V)

D<0>

 


Test Results: DFT from Cadence

dft(v("/vout" ?result "tran") 0 640n 64 "Rectangular" 1 "default")




 Matlab: Output Waveform reconstructed from sampled data



Matlab:

 Output spectrum using DFT (from $N = 1 \rightarrow 33$)




(3)

Using VerilogA Blocks

(Using “Clocked Comparators” VerilogA Blocks)


4-bit Flash ADC & DAC

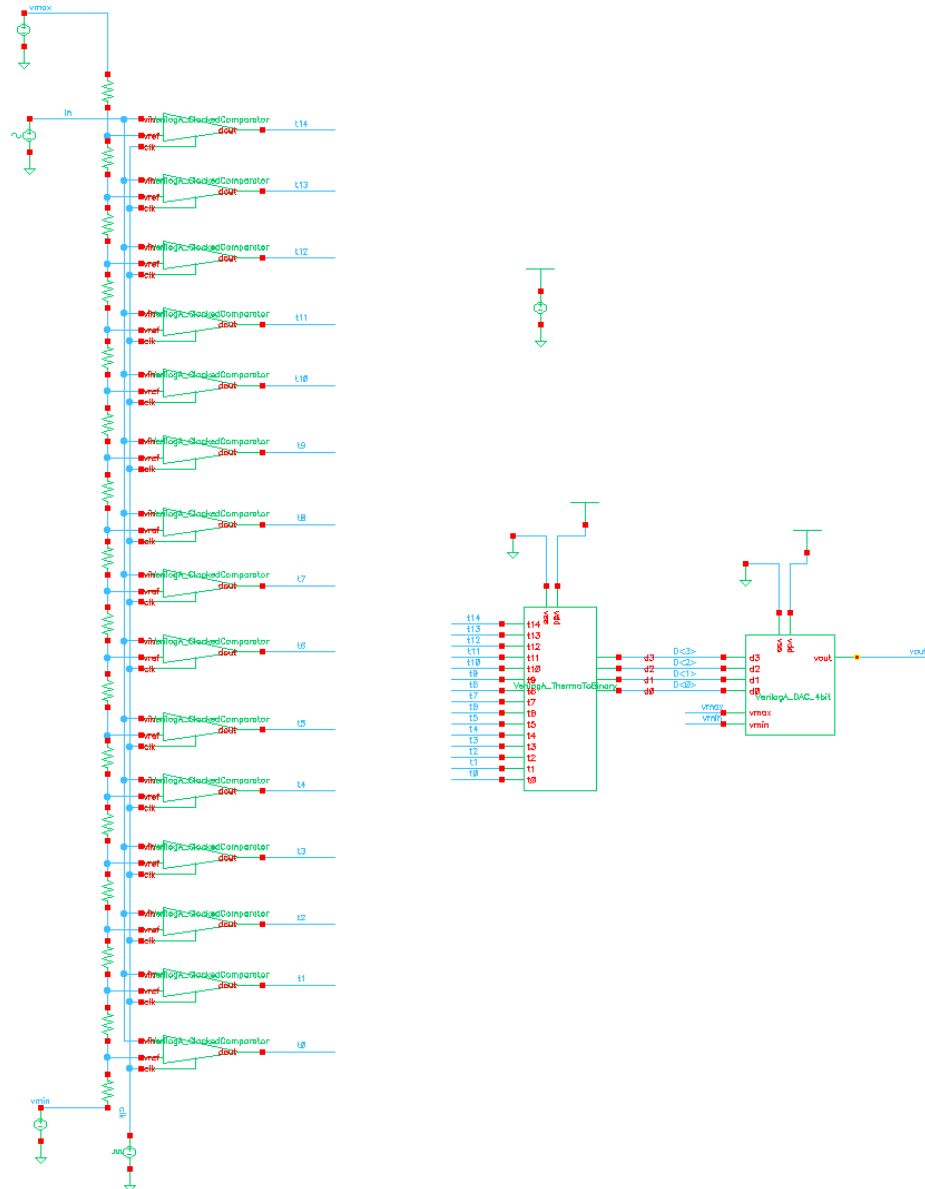

Test Results: Analog Waveforms


Transient Response

Sat Feb 24 15:49:58 2018

 

Test Results:

Thermometer Outputs from Comparators

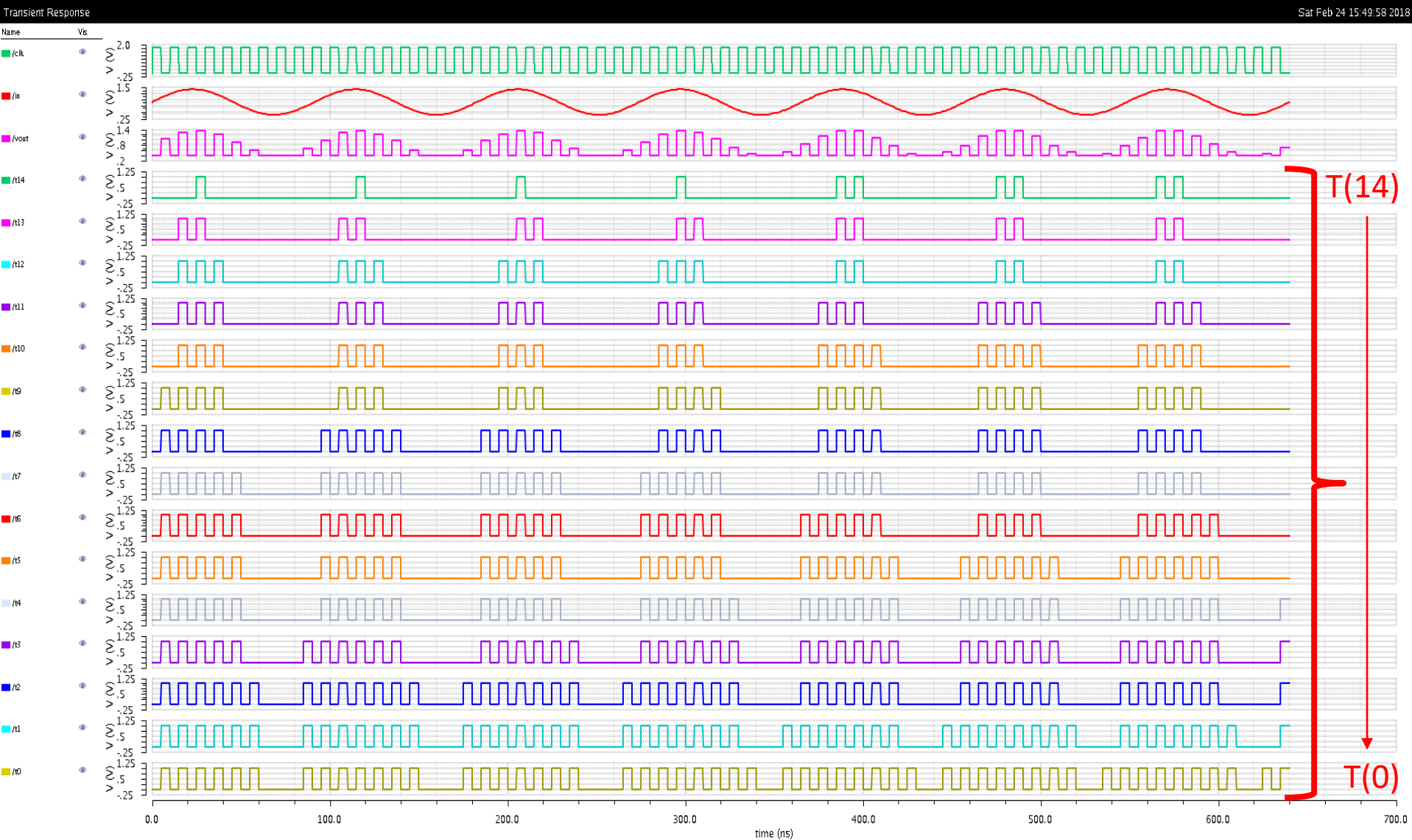

Test Results:


Digital Outputs from Encoder

Transient Response

Name


v / D<3>; tan (V)

D<3>

 


v / D<2>; tan (V)

D<2>

 


v / D<1>; tan (V)

D<1>

 

v / D<0>; tan (V)

D<0>

 

0.0 100.0 200.0 300.0 400.0 500.0 600.0 700.0


time (ns)

Test Results: DFT from Cadence


dft(v("/vout" ?result "tran") 0 640n 64 "Rectangular" 1 "default")



 Matlab: Output Waveform reconstructed from sampled data



 Matlab: Output spectrum using DFT (from $N = 1 \rightarrow 33$)





Matlab & VerilogA Codes

VerilogA: Clocked Comparator

```
// VerilogA for ADC_Ideal_4bit_FlashADC, VerilogA_ClockedComparator, veriloga

`include "constants.vams"
`include "disciplines.vams"

module VerilogA_ClockedComparator(dout,vref,vin,clk);

parameter real clk_th=0.9;
parameter real delay = 0;
parameter real ttime = 1p;

input vin,vref,clk;
output dout;

electrical dout,vref,vin,clk;
real d_result;

analog begin

    @(cross(V(clk) - clk_th, -1)) begin
        if(V(vin) > V(vref)) begin
            d_result = 1;
        end
        else begin
            d_result = 0;
        end
    end

    @(cross(V(clk) - clk_th, +1)) begin
        d_result = 0;
    end

    V(dout) <+ transition(d_result,delay,ttime);

end
endmodule
```

VerilogA:

Resistive Ladder & Comparators

{1}

```
// VerilogA for ADC_Ideal_4bit_FlashADC, VerilogA_LadderAndComparators, veriloga
```

```
`include "constants.vams"
`include "disciplines.vams"
```

```
module
VerilogA_LadderAndComparators(vin,clk,vmax,vmin,t0,t1,t2,t3,t4,t5,t6,t7,t8,t9,t10,t11,t12,t13,t14);
```

```
parameter real vtrans=0.5;
parameter real delay = 0;
parameter real ttime = 1p;
parameter real clk_threshold = 0.9;           //vdd is 1.8v
```

```
input clk,vin,vmin,vmax;
output t0,t1,t2,t3,t4,t5,t6,t7,t8,t9,t10,t11,t12,t13,t14;
```

```
electrical vin,vmin,vmax,clk;
electrical t0,t1,t2,t3,t4,t5,t6,t7,t8,t9,t10,t11,t12,t13,t14;
real step,t_0,t_1,t_2,t_3,t_4,t_5,t_6,t_7,t_8,t_9,t_10,t_11,t_12,t_13,t_14;
```

```
analog begin
```

```
    step = (V(vmax)-V(vmin))/16;
```

```
    // Sampling Phase (-1 is for falling edge)
```

```
    @(cross(V(clk) - clk_threshold, -1))
```

```
    begin
```

```
        if (V(vin) > step+V(vmin))
            t_0 = 1;
```

```
        else
            t_0 = 0;
```

```
        if (V(vin) > ((2*step)+V(vmin)))
            t_1 = 1;
```

```
        else
            t_1 = 0;
```

```
        if (V(vin) > ((3*step)+V(vmin)))
            t_2 = 1;
```

```
        else
            t_2 = 0;
```

```
        if (V(vin) > ((4*step)+V(vmin)))
            t_3 = 1;
```

```
        else
            t_3 = 0;
```

```
        if (V(vin) > ((5*step)+V(vmin)))
            t_4 = 1;
```

```
        else
            t_4 = 0;
```

```
        if (V(vin) > ((6*step)+V(vmin)))
            t_5 = 1;
```

```
        else
            t_5 = 0;
```

```
        if (V(vin) > ((7*step)+V(vmin)))
            t_6 = 1;
```

```
        else
            t_6 = 0;
```

```
        if (V(vin) > ((8*step)+V(vmin)))
            t_7 = 1;
```

```
        else
            t_7 = 0;
```

```
        if (V(vin) > ((9*step)+V(vmin)))
            t_8 = 1;
```

```
        else
            t_8 = 0;
```

VerilogA:

Resistive Ladder & Comparators

{2}
Cont'd

```
        if (V(vin) > ((10*step)+V(vmin)))
            t_9 = 1;
        else
            t_9 = 0;

        if (V(vin) > ((11*step)+V(vmin)))
            t_10 = 1;
        else
            t_10 = 0;

        if (V(vin) > ((12*step)+V(vmin)))
            t_11 = 1;
        else
            t_11 = 0;

        if (V(vin) > ((13*step)+V(vmin)))
            t_12 = 1;
        else
            t_12 = 0;

        if (V(vin) > ((14*step)+V(vmin)))
            t_13 = 1;
        else
            t_13 = 0;

        if (V(vin) > ((15*step)+V(vmin)))
            t_14 = 1;
        else
            t_14 = 0;

    end
```

```
        @(cross(V(clk) - clk_threshold, +1))
        begin
            t_0 = 0;          t_1 = 0;          t_2 = 0;
            t_3 = 0;          t_4 = 0;          t_5 = 0;
            t_6 = 0;          t_7 = 0;          t_8 = 0;
            t_9 = 0;          t_10 = 0;         t_11 = 0;
            t_12 = 0;         t_13 = 0;         t_14 = 0;
        end

        V(t0) <+ transition(t_0,delay,ttime);
        V(t1) <+ transition(t_1,delay,ttime);
        V(t2) <+ transition(t_2,delay,ttime);
        V(t3) <+ transition(t_3,delay,ttime);
        V(t4) <+ transition(t_4,delay,ttime);
        V(t5) <+ transition(t_5,delay,ttime);
        V(t6) <+ transition(t_6,delay,ttime);
        V(t7) <+ transition(t_7,delay,ttime);
        V(t8) <+ transition(t_8,delay,ttime);
        V(t9) <+ transition(t_9,delay,ttime);
        V(t10) <+ transition(t_10,delay,ttime);
        V(t11) <+ transition(t_11,delay,ttime);
        V(t12) <+ transition(t_12,delay,ttime);
        V(t13) <+ transition(t_13,delay,ttime);
        V(t14) <+ transition(t_14,delay,ttime);

    end

endmodule
```

VerilogA:

Thermometer-To-Binary Encoder

```
// VerilogA for ADC_Class, ThermometerToBinary, veriloga
```

```
`include "constants.vams"
`include "disciplines.vams"
```

```
module
ThermometerToBinary(t0,t1,t2,t3,t4,t5,t6,t7,t8,t9,t10,t11,t12,t13,t14,d0,d1,d2,d3,vdd,vss
);
```

```
parameter real vtrans=0.5;
parameter real delay = 0;
parameter real ttime = 1p;
```

```
inout vdd,vss;
input t0,t1,t2,t3,t4,t5,t6,t7,t8,t9,t10,t11,t12,t13,t14;
output d0,d1,d2,d3;
```

```
electrical vdd,vss;
electrical t0,t1,t2,t3,t4,t5,t6,t7,t8,t9,t10,t11,t12,t13,t14;
electrical d0,d1,d2,d3;
```

```
real d_0,d_1,d_2,d_3;
real vmid;
```

```
//My inputs are from 0 to Vdd, My outputs are from 0 to 1 (binary codes)
```

```
analog begin
```

```
vmid = (V(vdd)+V(vss))/2;
```

```
if (V(t14)>0.9) begin
d_3 = 1; d_2 = 1; d_1 = 1; d_0 = 1; end
```

```
else if (V(t13)>0.9) begin
d_3 = 1; d_2 = 1; d_1 = 1; d_0 = 0; end
```

```
else if (V(t12)>0.9) begin
d_3 = 1; d_2 = 1; d_1 = 0; d_0 = 1; end
```

```
else if (V(t11)>0.9) begin
d_3 = 1; d_2 = 1; d_1 = 0; d_0 = 0; end
```

```
else if (V(t10)>0.9) begin
d_3 = 1; d_2 = 0; d_1 = 1; d_0 = 1; end
```

```
else if (V(t9)>0.9) begin
d_3 = 1; d_2 = 0; d_1 = 1; d_0 = 0; end
```

```
else if (V(t8)>0.9) begin
d_3 = 1; d_2 = 0; d_1 = 0; d_0 = 1; end
```

```
else if (V(t7)>0.9) begin
d_3 = 1; d_2 = 0; d_1 = 0; d_0 = 0; end
```

```
else if (V(t6)>0.9) begin
d_3 = 0; d_2 = 1; d_1 = 1; d_0 = 1; end
```

```
else if (V(t5)>0.9) begin
d_3 = 0; d_2 = 1; d_1 = 1; d_0 = 0; end
```

```
else if (V(t4)>0.9) begin
d_3 = 0; d_2 = 1; d_1 = 0; d_0 = 1; end
```

```
else if (V(t3)>0.9) begin
d_3 = 0; d_2 = 1; d_1 = 0; d_0 = 0; end
```

```
else if (V(t2)>0.9) begin
d_3 = 0; d_2 = 0; d_1 = 1; d_0 = 1; end
```

```
else if (V(t1)>0.9) begin
d_3 = 0; d_2 = 0; d_1 = 1; d_0 = 0; end
```

```
else if (V(t0)>0.9) begin
d_3 = 0; d_2 = 0; d_1 = 0; d_0 = 1; end
```

```
else begin
d_3 = 0; d_2 = 0; d_1 = 0; d_0 = 0; end
```

```
end
```

```
endmodule
```

```
else if (V(t10)>0.9) begin
d_3 = 1; d_2 = 0; d_1 = 1; d_0 = 1; end
else if (V(t9)>0.9) begin
d_3 = 1; d_2 = 0; d_1 = 1; d_0 = 0; end
else if (V(t8)>0.9) begin
d_3 = 1; d_2 = 0; d_1 = 0; d_0 = 1; end
else if (V(t7)>0.9) begin
d_3 = 1; d_2 = 0; d_1 = 0; d_0 = 0; end
else if (V(t6)>0.9) begin
d_3 = 0; d_2 = 1; d_1 = 1; d_0 = 1; end
else if (V(t5)>0.9) begin
d_3 = 0; d_2 = 1; d_1 = 1; d_0 = 0; end
else if (V(t4)>0.9) begin
d_3 = 0; d_2 = 1; d_1 = 0; d_0 = 1; end
else if (V(t3)>0.9) begin
d_3 = 0; d_2 = 1; d_1 = 0; d_0 = 0; end
else if (V(t2)>0.9) begin
d_3 = 0; d_2 = 0; d_1 = 1; d_0 = 1; end
else if (V(t1)>0.9) begin
d_3 = 0; d_2 = 0; d_1 = 1; d_0 = 0; end
else if (V(t0)>0.9) begin
d_3 = 0; d_2 = 0; d_1 = 0; d_0 = 1; end
else begin
d_3 = 0; d_2 = 0; d_1 = 0; d_0 = 0; end
```

```
V(d3) <+ transition(d_3,delay,ttime);
```

```
V(d2) <+ transition(d_2,delay,ttime);
```

```
V(d1) <+ transition(d_1,delay,ttime);
```

```
V(d0) <+ transition(d_0,delay,ttime);
```

```
end
```

```
endmodule
```

VerilogA: 4-bit DAC

```
// VerilogA for ADC_Ideal_4bit_FlashADC, VerilogA_DAC_4bit, veriloga

`include "constants.vams"
`include "disciplines.vams"

module VerilogA_DAC_4bit(d0,d1,d2,d3,vout,vdd,vss,vmin,vmax);

parameter real vtrans=0.5;
parameter real delay = 0;
parameter real ttime = 1p;

inout vdd,vss;
input d0,d1,d2,d3;
input vmin, vmax;
output vout;

electrical vout,vdd,vss,d0,d1,d2,d3,vmin,vmax;

real result,d_0,d_1,d_2,d_3;

analog begin
    d_3 = V(d3)*8;
    d_2 = V(d2)*4;
    d_1 = V(d1)*2;
    d_0 = V(d0)*1;

    result = ((d_3+d_2+d_1+d_0) * ((V(vmax)-V(vmin))/(16))) + V(vmin) ;

    V(vout) <+ transition(result,delay,ttime);

end

endmodule
```

Matlab Code: for DFT

```
clc; close all;
%data = importdata('verilogA_DAC_output.csv');
data = importdata('ideal_DAC_output.csv');
t = data(:,1);
x = data(:,2);
plot(t,x,'linewidth',2); grid on;
xlabel('time(s)'); ylabel('Voltage(V)')
```

```
FS = 1;
fs = 100e6;
fnyquist = fs/2;
N = 64;
cycles = 7;
fx = (cycles/N)*fs;
Afs = 1;
```

```
% spectrum
% PrettyFFT Gives ENOB, SNDR, SFDR, SNR
figure
prettyFFT(x); grid on;
```

```
figure
s = abs(fft(x,N))
s = s + 1e-7
p = s(1:(N/2)+1);
p = 2*p/N/FS;
f = [0:(N/2)]
stem(f,p,'linewidth',2); grid on;
```

```
figure
f = [0:N-1]
s = 20*log10(2*s/N/FS)
plot(f,s,'linewidth',2); grid on;
xlabel('frequency[bin]'); ylabel('DFT magnitude [dBFS]')
```

```
figure
m = s(1:(N/2)+1);
f = [0:(N/2)]
plot(f,m,'linewidth',2); grid on;
xlabel('frequency[bin]'); ylabel('DFT magnitude [dBFS]')
```